

NUC970B Application CKT for Random Power up Fail Issue


Dec. 30, 2015

Nuvoton Technology Corp.



Root Cause

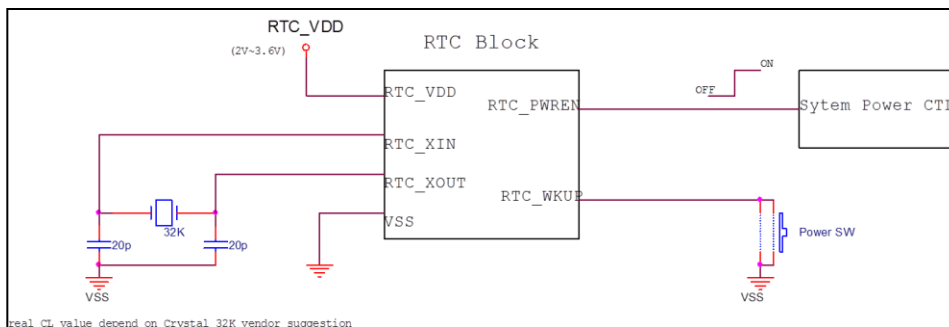- About NUC970B random power up failure issue, that is power-on latch miss by a little probability when powered directly. This issue can be avoided with NUC970's RTC power-on/off controller ◦ (as below figure)



Pin Name	I/O type	Brief
RTC_XIN (32768Hz)	I	32768Hz Crystal Input
RTC_XOUT (32768Hz)	O	32768Hz Crystal Output
RTC_WAKE	I	Wakeup Enable, Input, Low Active
RTC_PWREN	O	Power Enable
RTC_VDD	P	RTC Core, I/F & 32768Hz Crystal Power



- If power-on/off directly still is need by system design, Nuvoton provided two solutions for reference, please refer to the following pages ◦


Solution-1, Power Supervisor with WDT

- By power-on/off control directly and quickly, that is the safest way to use WDT (watchdog timer) for system power supervisors ◦
- The following of figure block shown the implement way.


Note. disadvantage, WDT part cost & one GPIO

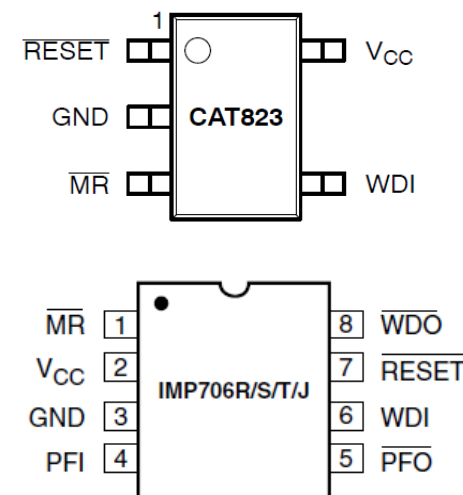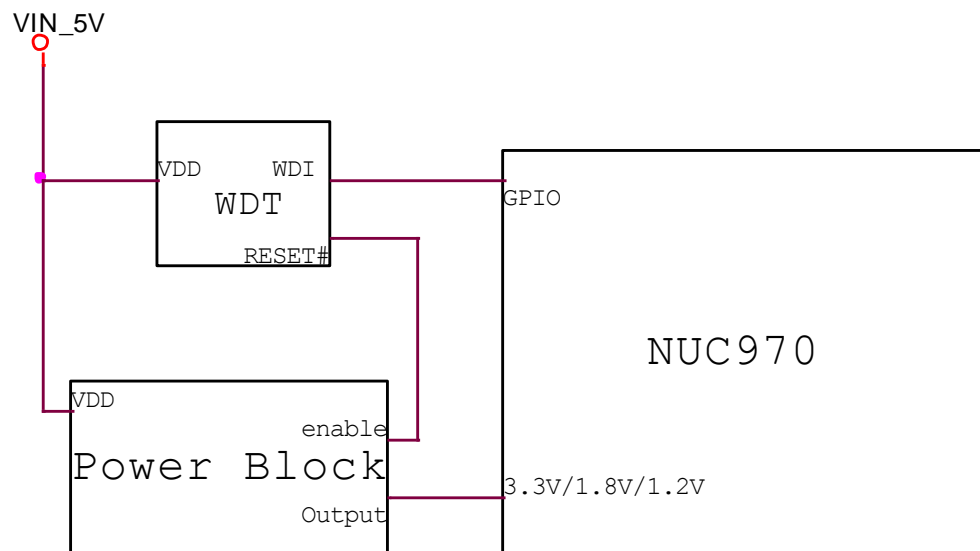About WDT IC selection, CAT823 & IMP706R are fine



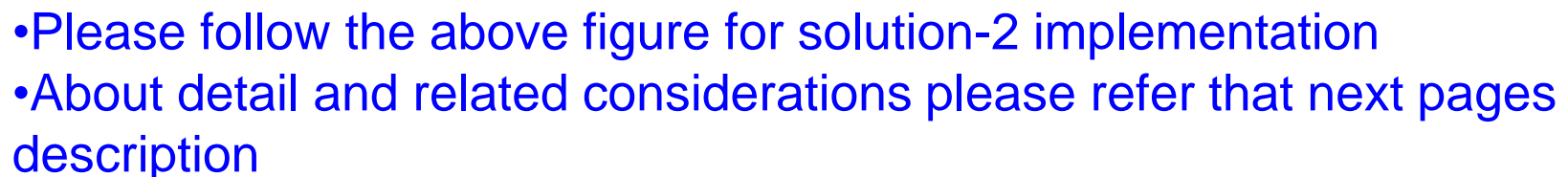


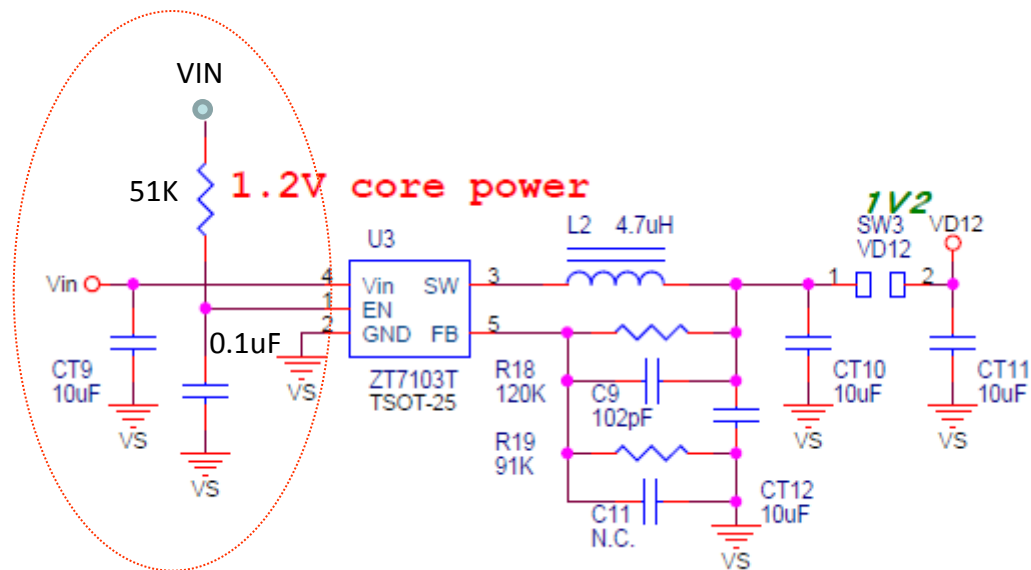For Power Sequence Issue, Coe Power Delay with R, C




Application CKT

(DC-DC with Hi level enable)



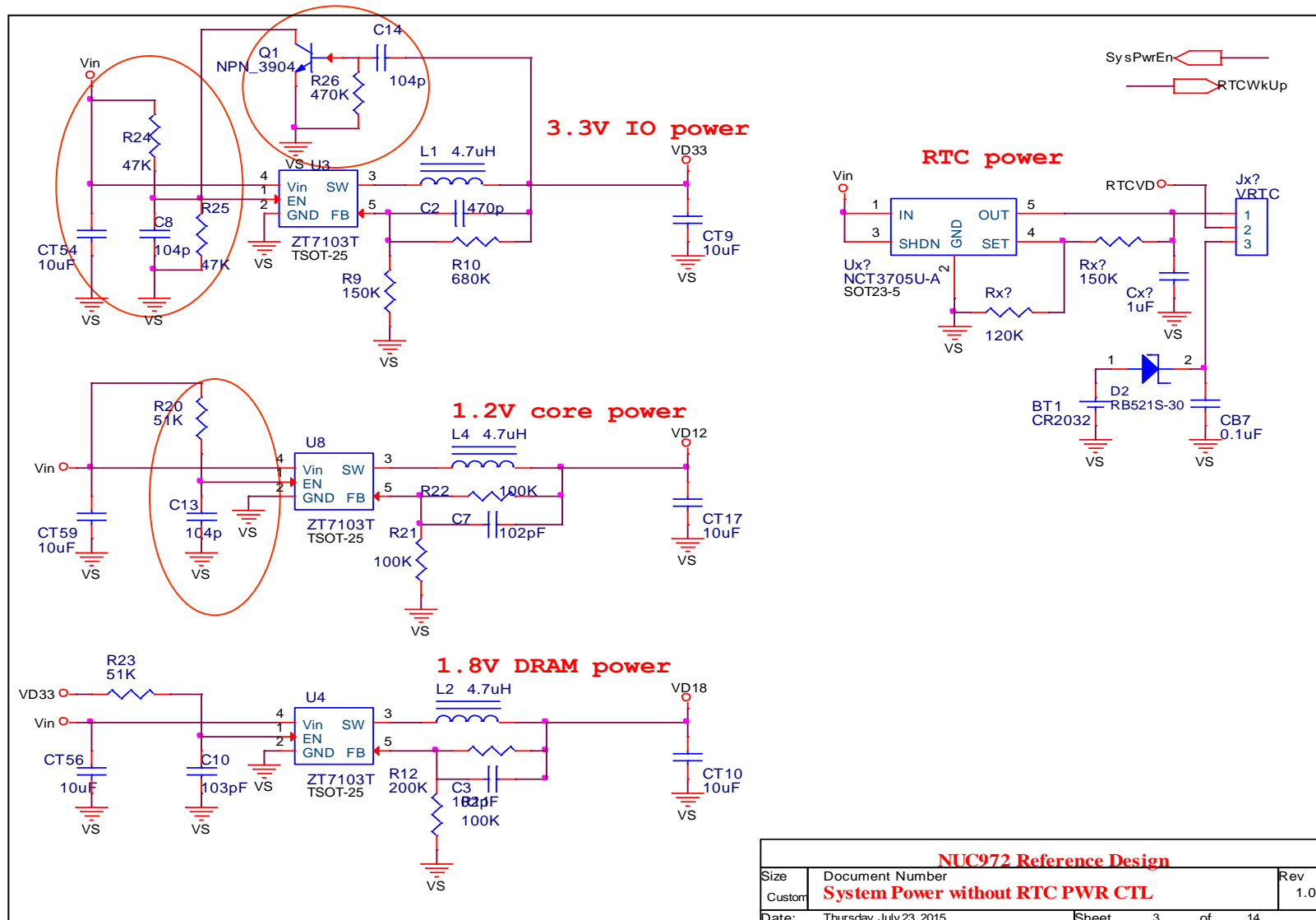


NUC972 Reference Design		
Size	Document Number	Rev
Custom	System Power without RTC PWR CTL	1.0
Date:	Thursday, July 23, 2015	Sheet 3 of 14

we innovate
nuvoTon

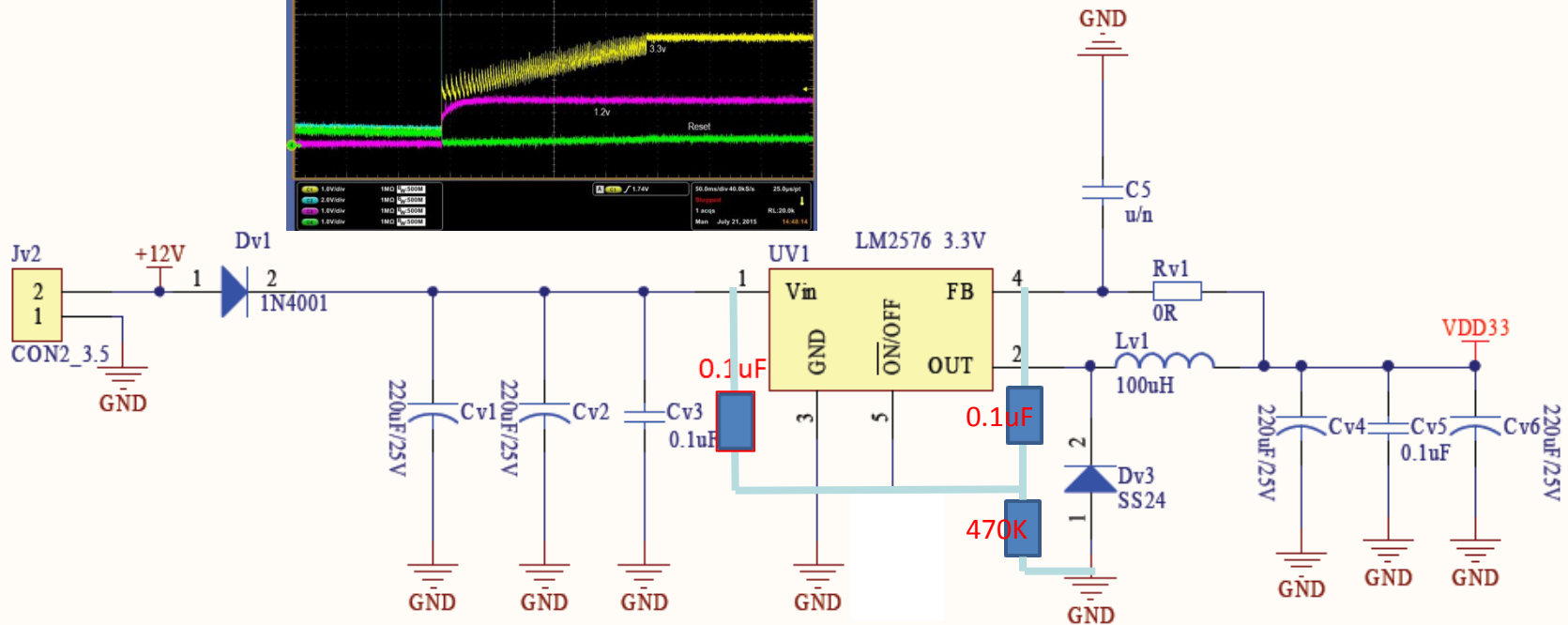

Application CKT with LDO

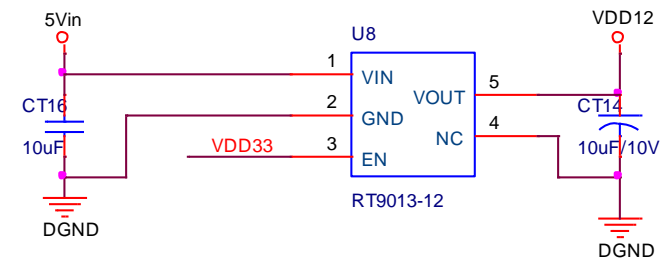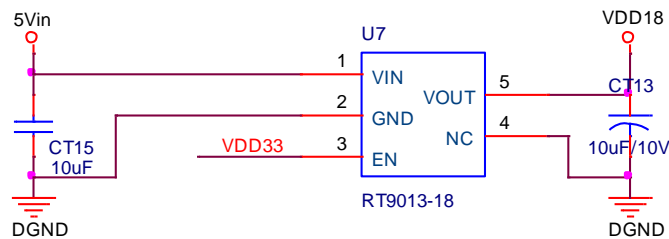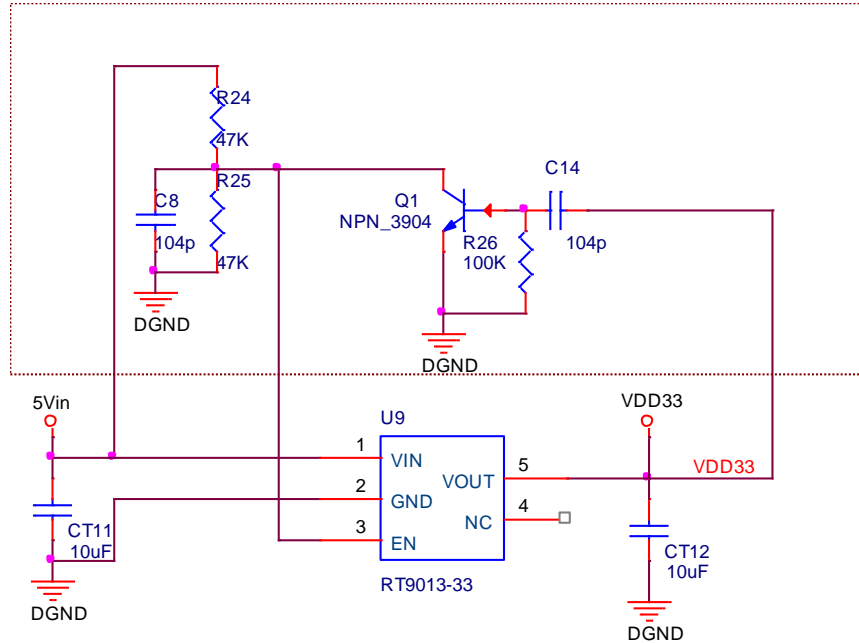


Description

- The CKT purpose, generates a ring oscillation waveform while power up period for POR (Power-on RESET) can latch correctly when I/O power was rose at 1.9V around
- It is robustness for long time and reliability test


Power up Successful Waveform with DC-DC

POR@1.9V

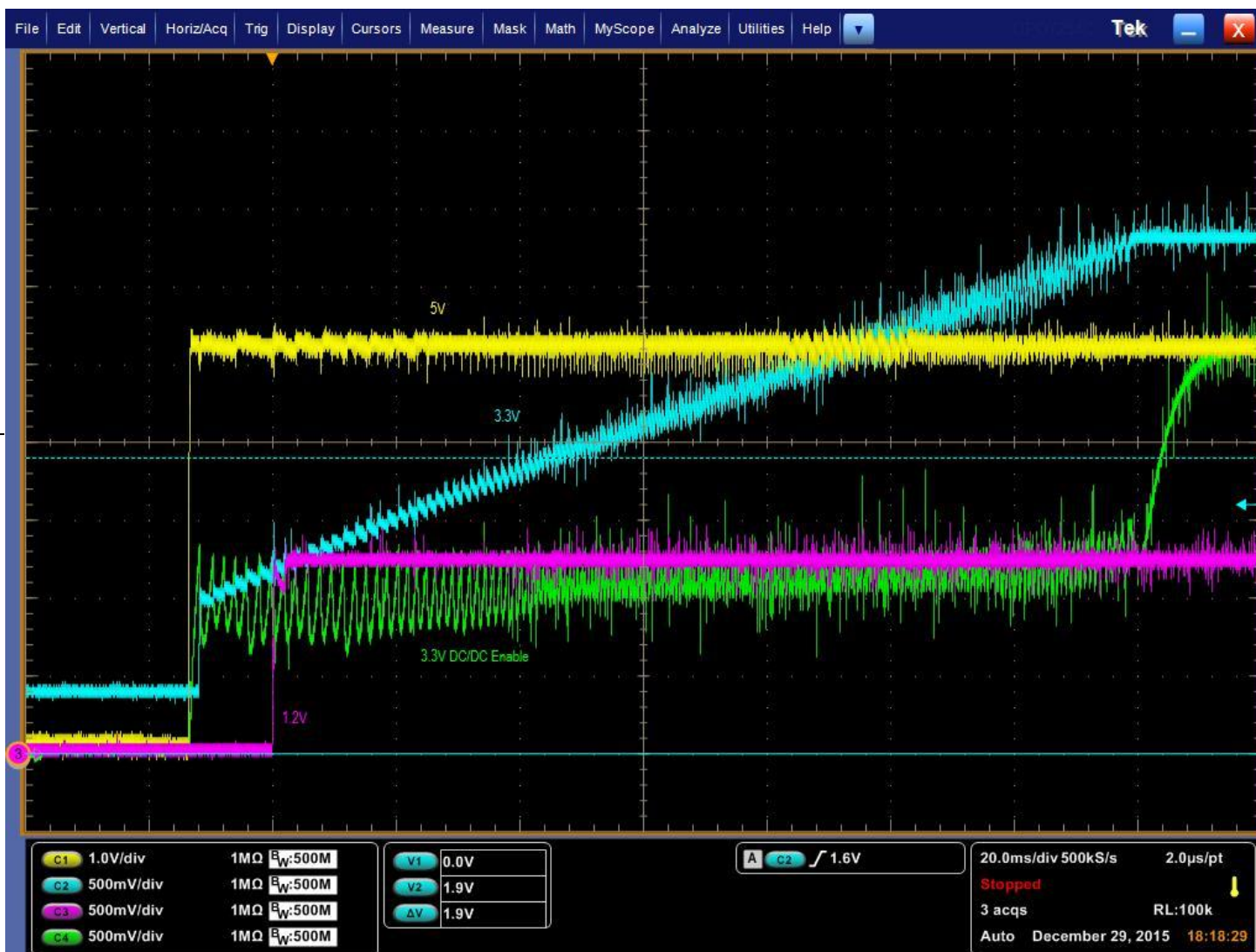


Power up Successful Waveform with LDO

POR@1.9V

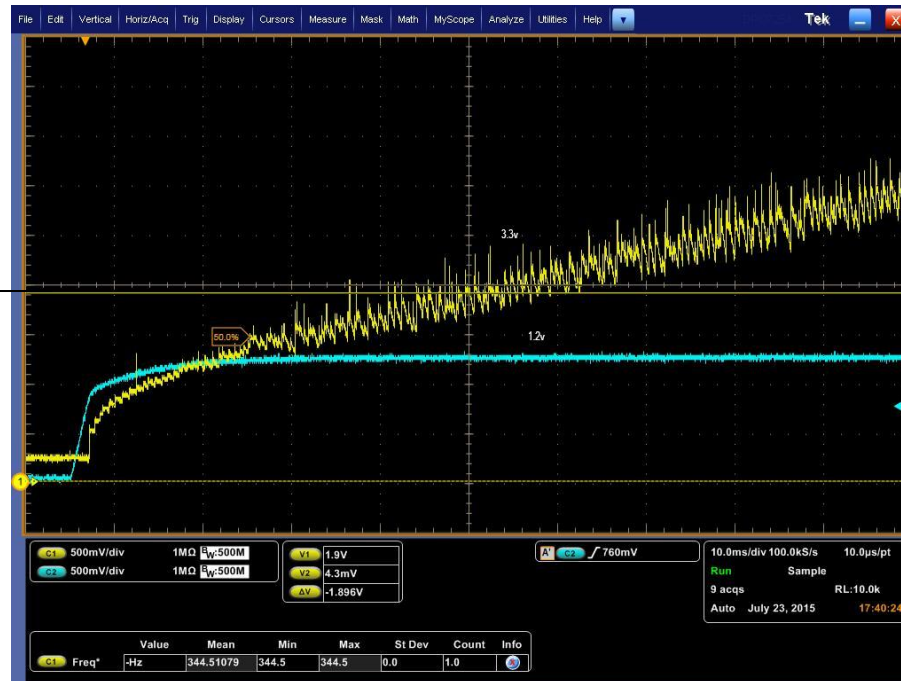

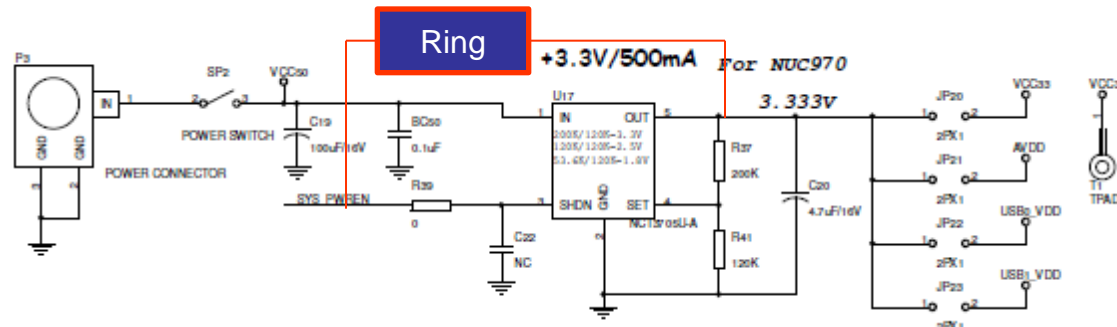Note. Ring block is same as DC-DC modification



Inner POR Behavior

- POR@1.9V can be active for many times by power up ring, it could make sure power-on latch successful for very time.

Note. LVR doesn't relate with power up, the behavior could be ignored.

