

nuvoTon

NUC970

Power Sequence & RESET



Nuvoton Technology Corp.

Process Concerns

- In standard IO, different voltages are supplied to the pre-driver (lower voltage) and post-driver (higher voltage).
- Because of the multi-power ESD (Electro Static Discharge) structure, there is a parasitic forward diode path from core power rail.
- I/O power rail (VD33) as shown in Fig.3 the diode in red, if the core (lower) voltage is powered up earlier than the I/O (higher) voltage without care, there will be current flowing through the parasitic diode that may trigger latch-up.
- So user should to avoid this problem occurring, when system power up/down.

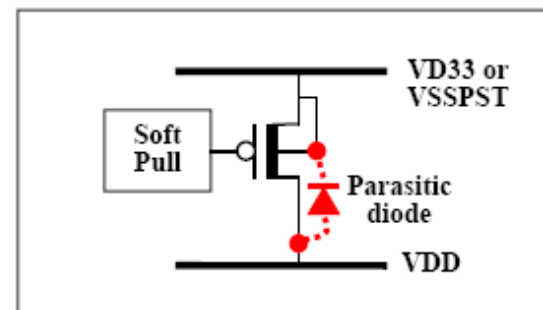


Fig. 3 Parasitic diode between core and I/O power rails

Power Up/Down Sequence

- Power Up sequence

- Higher Voltage (3.3V) is early than MVDD (1.8V) and Core(1.2V)
- Sequence: $T_{33} \geq T_{18} \geq T_{12}$
- The time delay gap T_{33} with T_{12} , less than 1mS is recommend
- The time delay gap T_{18} with T_{12} , 0mS is recommend


- Power Down Sequence

- The lower voltage (1.2V) should be powered down first and then the higher one (3.3V)
- Sequence: $T_{12} \geq T_{18} \geq T_{33}$

Note.

- T_{12} means 1.2V powered time for Core & PLL
- T_{18} means 1.8V powered time for MVDD
- T_{33} means 3.3V powered time for digital IO and analog IO


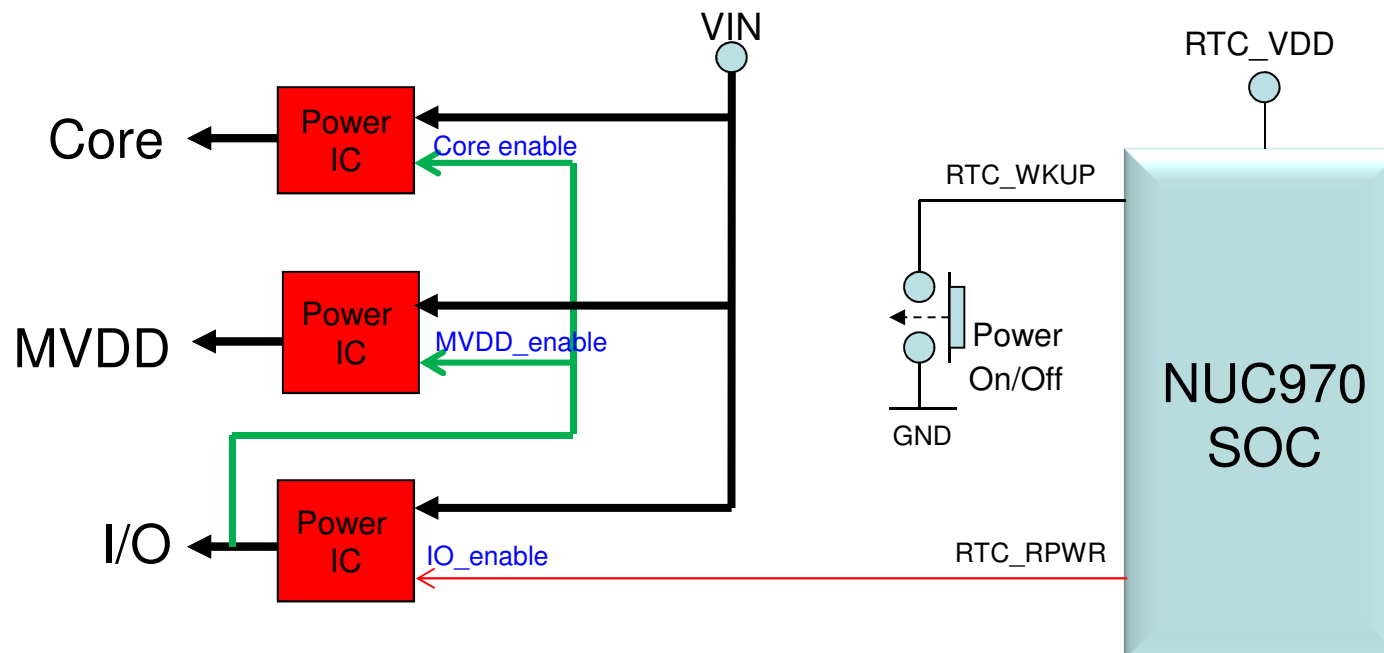
Recommended Connection for Power IC enable CTL of IO, MVDD & Core




NUC970 RESET CKT

- Except for typical R,C to RESET, NUC970 series also need an auxiliary circuit as the figure.
- It is robust for system reset when power on/off quickly or the power on sequence time of Core Power is too late than IO power.


Reset robustness CKT

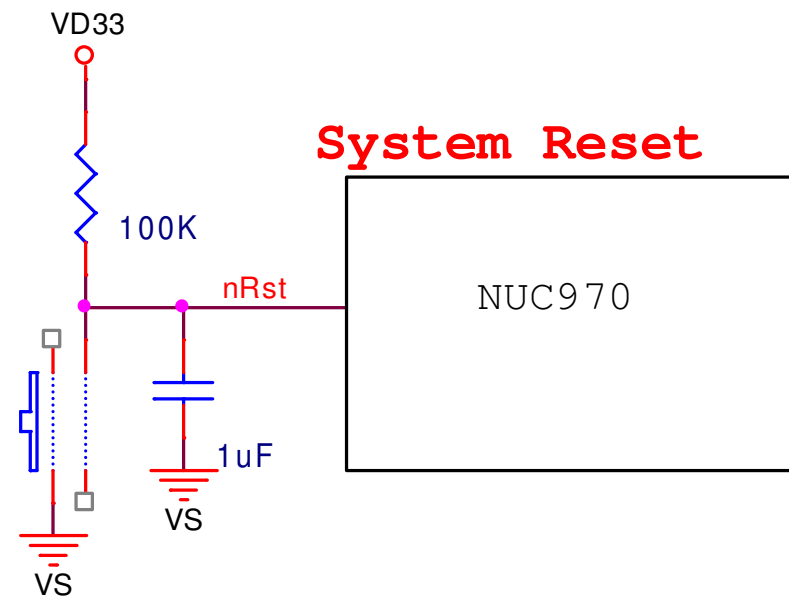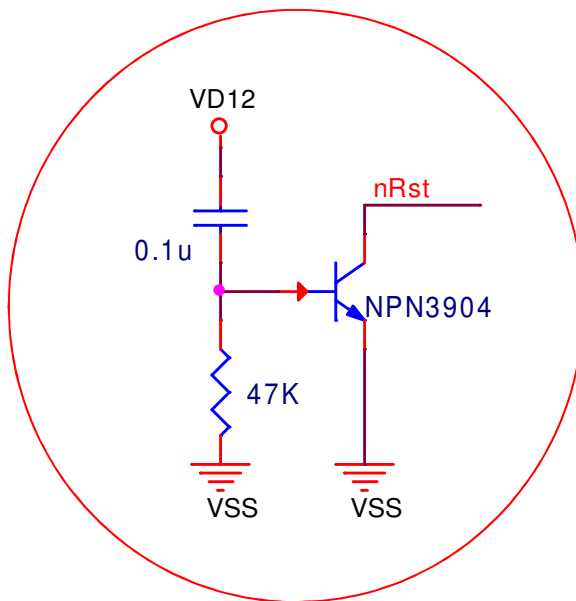

Power Sequence with RESET

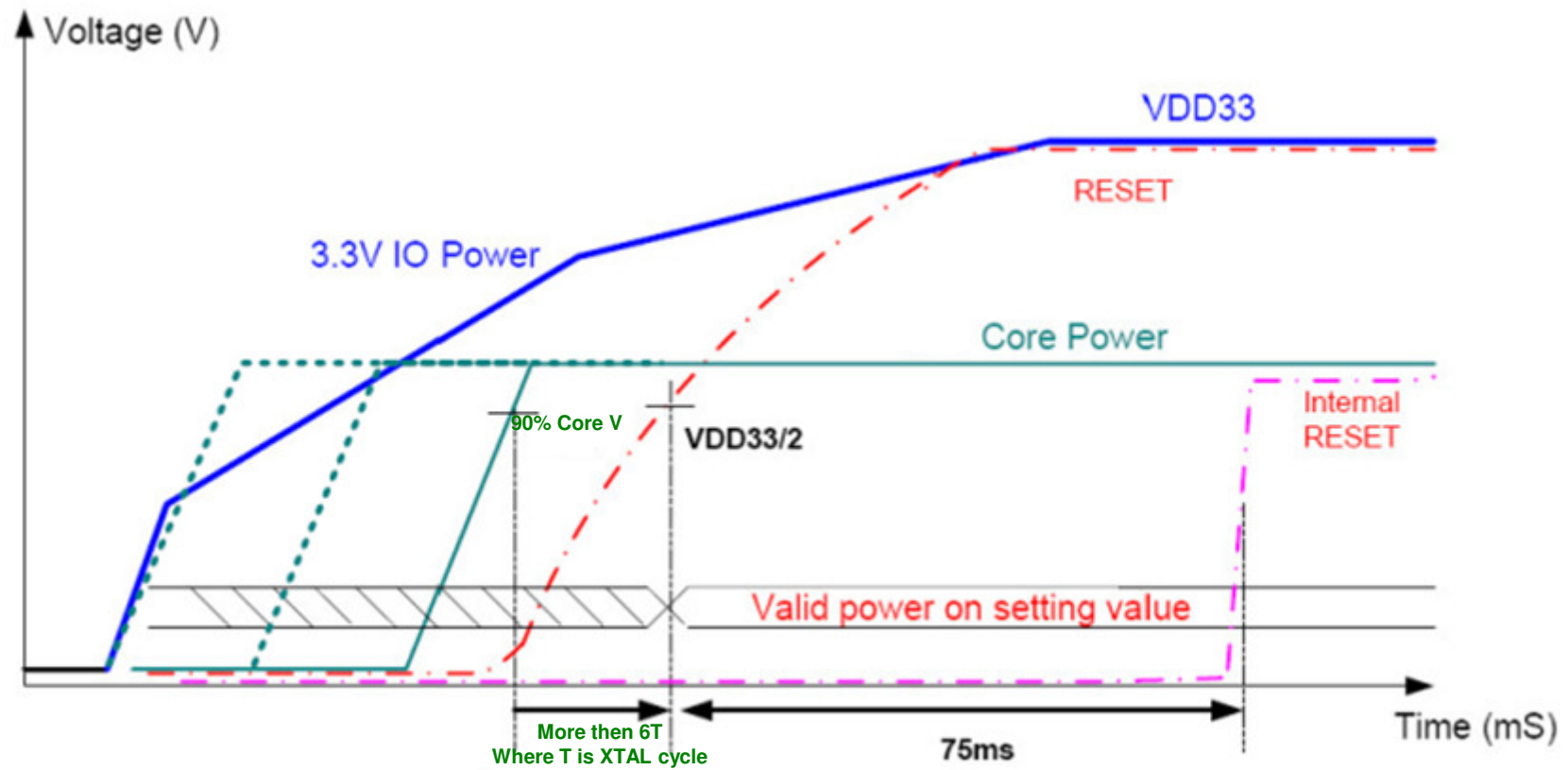

RESET Waveform Example

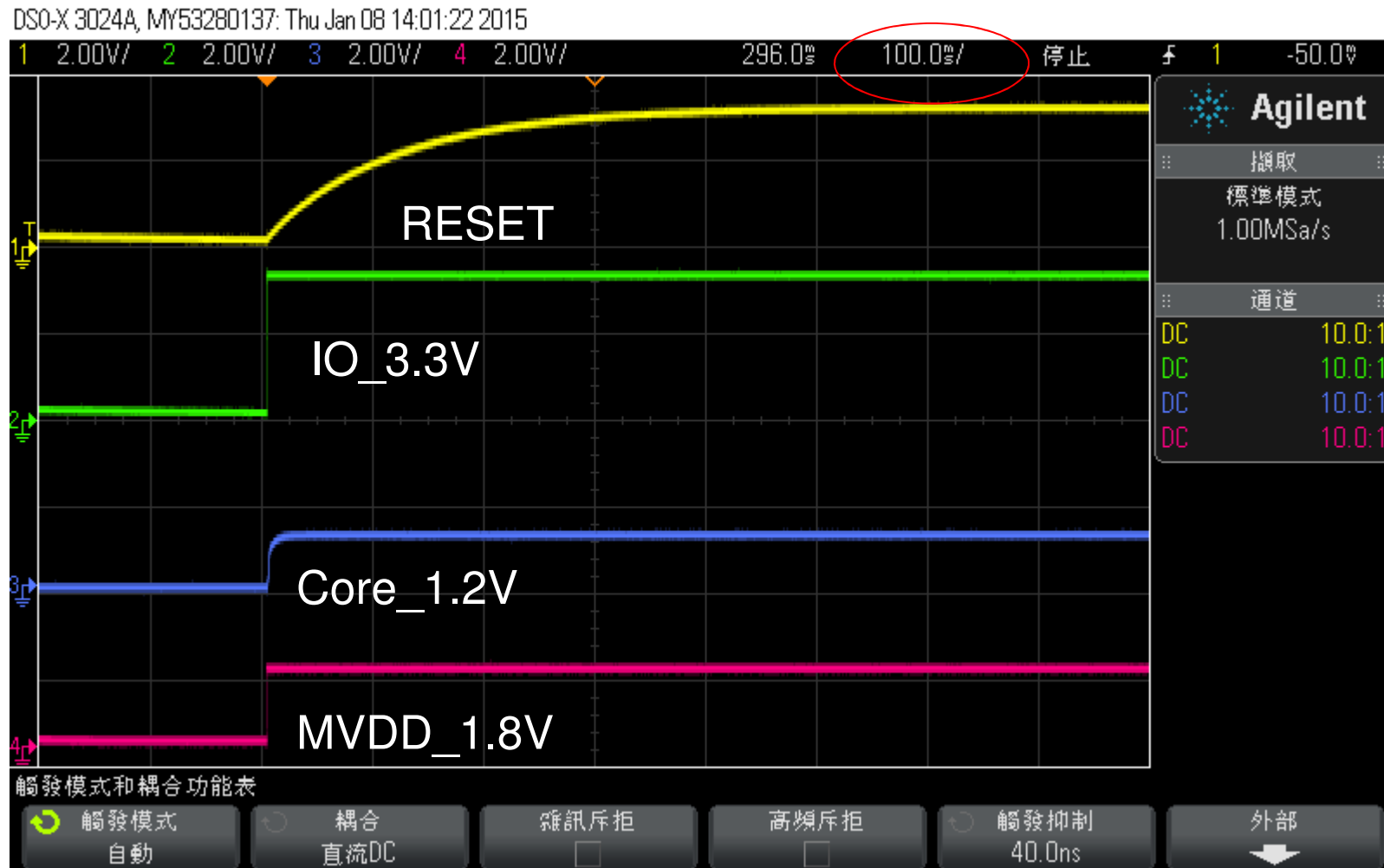

Power Sequence Relationship with RTC

